# ELECTRICITY 10 DAY LESSION PLAN

The following 15 Blue Prints are to be drawn in the schematic form using the techniques learned in class.

You are required to have the following items present on each schematic.

- 1. Power labeled
- 2. Straight lines
- 3. Proper color code on all lines
- 4. Proper devices drawn
- 5. Boxes around all devices

You can refer to the following videos for help:

- SinglePole
   https://www.youtube.com/watch?v=CaaLw01fMo8
   &t=2s
- 3way
   https://www.youtube.com/watch?v=xBEi\_fYDMJw
- 4ways https://www.youtube.com/watch?v=jYFVsUqY6zc

- Receptacle https://www.youtube.com/watch?v=xex8cPv8CtA
- GFCI https://www.youtube.com/watch?v=Fe9hwE8dN k

#### **NEAT.....NOT SLOPPY**

Here are the following deductions.


- 1. -3 for incorrect labeling for each infraction
- 2. -3 for unlabeled power source
- 3. -3 for missing boxes and connections outside of the box for each infraction
- 4. -5 for each device that would not work properly
- 5. A ZERO for projects not complete.

All 15 projects will be averaged into 1 cumulative grade!


Email if any questions. Brian.Oneill@DCCTC.org

Here are the following 15 projects!


Name	Date
Draw the circuit diagram of the	below architectural drawing, after approval
Wire the project!	

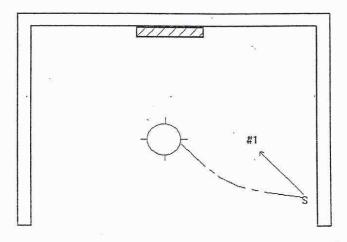


Name	Date
Draw the circuit diagram of the below archit Wire the project!	ectural drawing, after approval

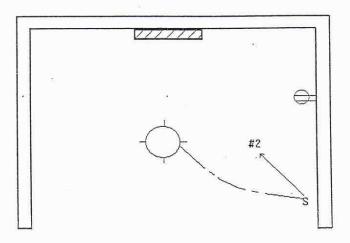


Name	Date
Draw the circuit diagram of the belowire the project !	w architectural drawing, after approval

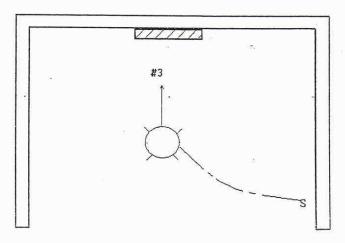


Name		Dat	e		
Draw the circuit diagram Wire the project!	of the below	architectural	drawing,	after	approval

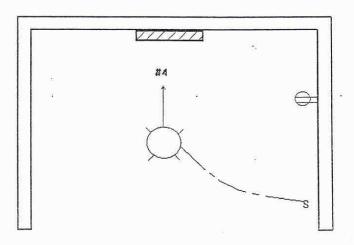


Name	Date
Draw the circuit diagram of the be Wire the project !	low architectural drawing, after approval

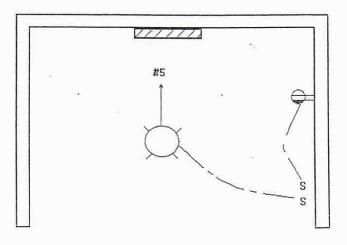


Name		nar	e		*
Draw the circuit diagram of Wire the project !	of the below	architectural	drawing,	after	approval

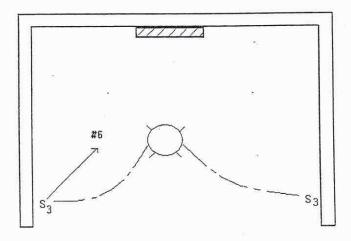

Name		Dat	e		
Draw the circuit diagram Wire the project !	of the below	architectural	drawing,	after	approval

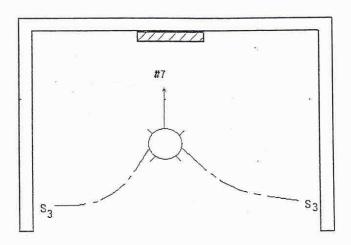

Name	Date
Draw the circuit diagram of the below arch	nitectural drawing, after approval
Wire the project!	

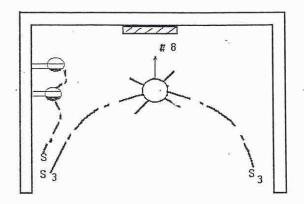


Name	Date
Draw the circuit diagram of the below arch	hitectural drawing, after approval
Wire the project!	

#9 S<sub>4</sub>

Name	Date
Draw the circuit diagram	of the below architectural drawing, after approval

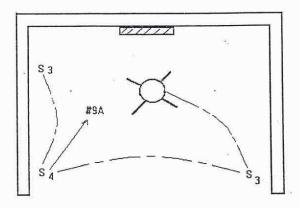Draw the circuit diagram of the below architectural drawing, after approval Wire the project!



Ivanic	Date
Draw the circuit diagram of the b	elow architectural drawing, after approval
Wire the project!	

#10

\$3

#10

\$3

#10

\$3

#10

\$3

#10

\$3

#10

\$3

#10

\$3


#10

#10


#10

#10


Name		Dat	e		-
Draw the circuit diagram of	f the belov	v architectural	drawing,	after	approval
Wire the project!					

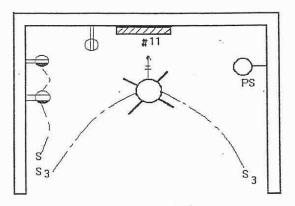

Name		Dat	e	
Draw the circuit diagram	of the below	architectural	drawing,	after approval
Wire the project!				

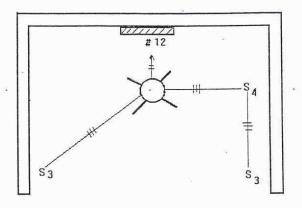

Name	Date
Draw the circuit diagram of the below	architectural drawing, after approval
Wire the project!	

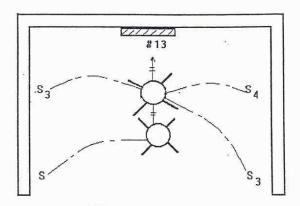

Name	Date
Draw the circuit diagram of the	below architectural drawing, after approval
Wire the project!	

#14

S DS